

## MileStone #1: Fixed-Frequency Waveform Generator

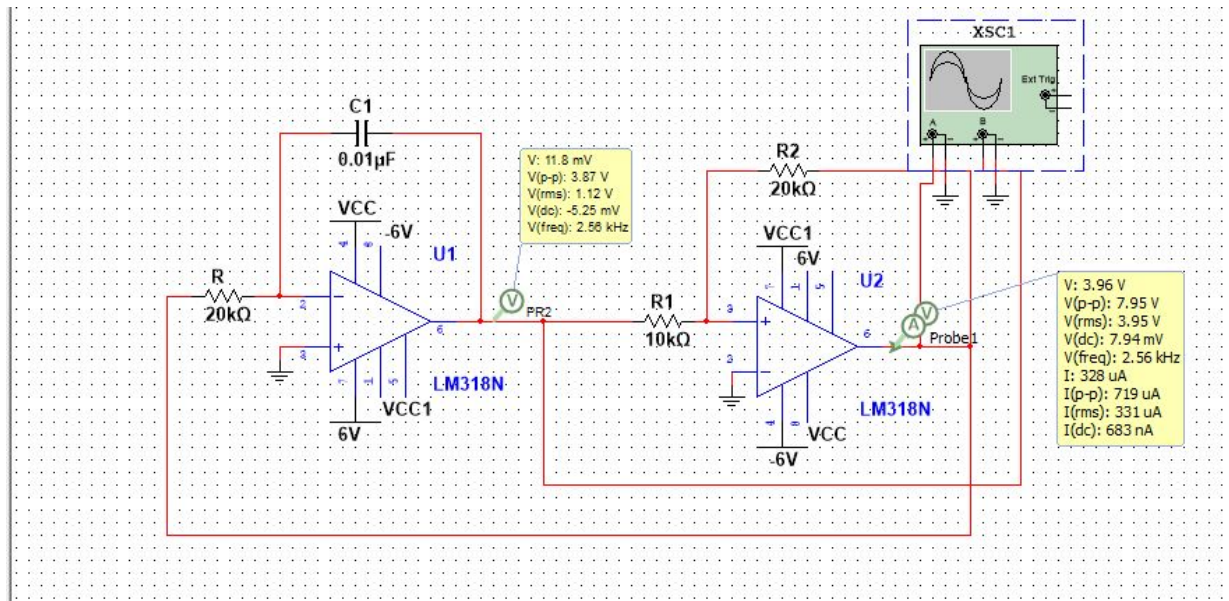


Figure 1: Circuit designed under test.

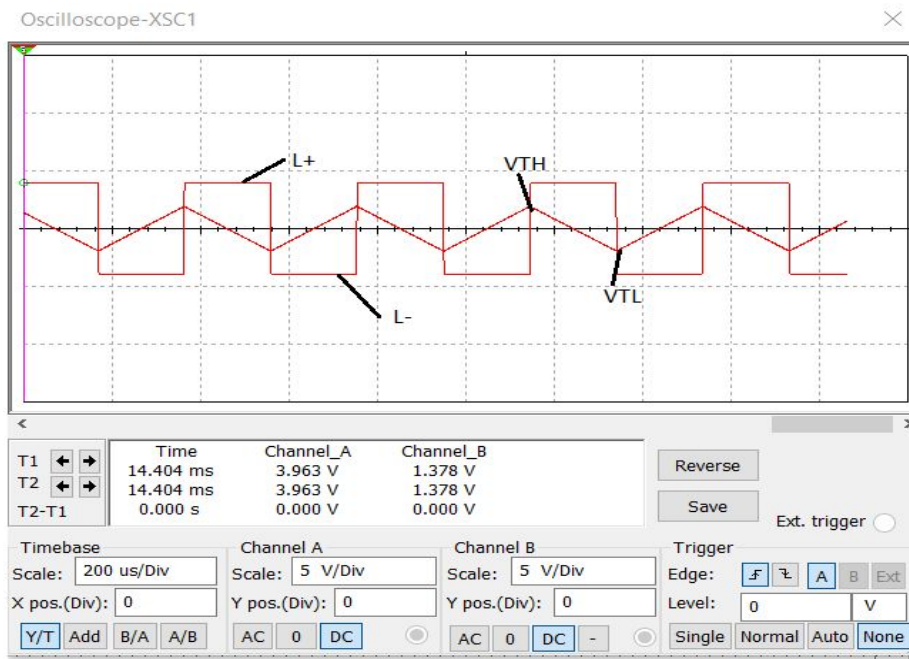


Figure 2: Waveforms Generated from Oscilloscope

- Channel A outputs the Square Waveform
- Channel B outputs the Triangular Waveform